

DAY – 1

IMPLEMENTATION OF AND GATE IN DATAFLOW MODEL.

VHDL CODE :

entity and_df is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end and_df;


architecture Dataflow of and_df is

begin

y <= a and b;

end Dataflow;

SCHEMATIC:

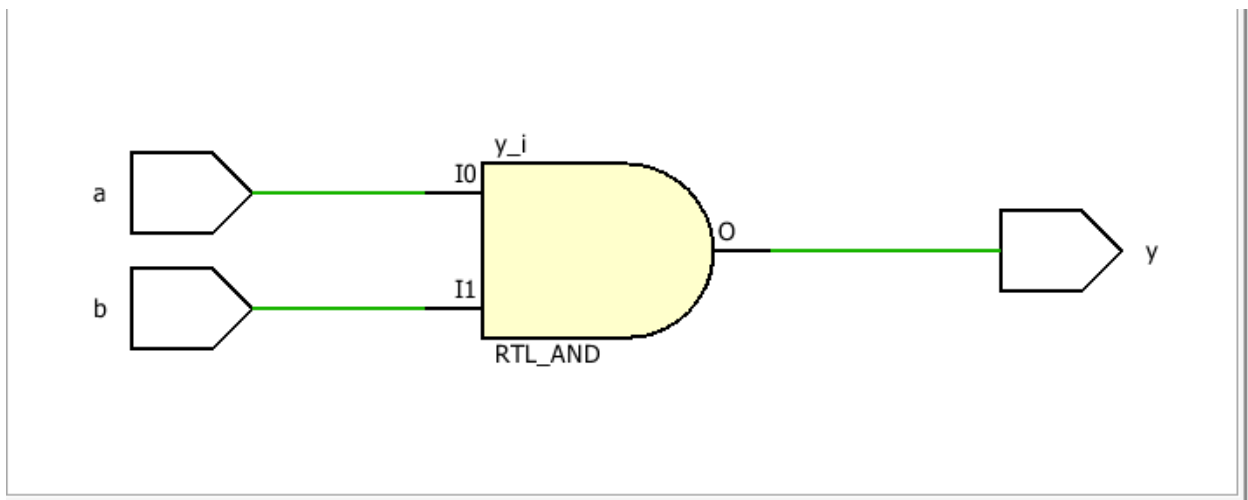

TBW CODE:

entity and_df_tb is

-- Port ();

end and_df_tb;

architecture Behavioral of and_df_tb is

component and_df is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end component;

signal a1:std_logic:='0';

signal b1:std_logic:='0';

signal y1:std_logic;

begin

uut:and_df port map(a=>a1,b=>b1,y=>y1);

stim_proc:process

begin

wait for 100 ns;

a1<='0';

b1<='1';

wait for 100 ns;

a1<='1';

b1<='0';

```
wait for 100 ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

WAVEFORM:

 

IMPLEMENTATION OF OR GATE IN DATAFLOW MODEL.

VHDL CODE:

```
entity or_df is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          y : out STD_LOGIC);
```

```
end or_df;
```


```
architecture Dataflow of or_df is
```

```
begin
```

```
y<= a or b;
```

```
end Dataflow;
```

SCHEMATIC:

 

TBW CODE :

```
entity or_df_tb is
```

```
-- Port ( );
```

```
end or_df_tb;
```

```
architecture Behavioral of or_df_tb is
```

```
component or_df is
```

```
Port ( a : in STD_LOGIC;
```

```
      b : in STD_LOGIC;
```

```
      y : out STD_LOGIC);
```

```
end component;
```

```
signal a1: std_logic := '0';
```

```
signal b1: std_logic := '0';
```

```
signal y1: std_logic;
```

```

begin

uut:or_df port map (a=>a1,b=>b1,y=>y1);

stim_proc:process

begin

wait for 100 ns;

a1<='0';

b1<='1';

wait for 100 ns;

a1<='1';

b1<='0';

wait for 100 ns;

a1<='1';

b1<='1';


wait;

end process;

end Behavioral;

```

WAVEFORM:

 

IMPLEMENTATION OF NOT GATE IN DATAFLOW MODEL

VHDL CODE:

entity NOTGATE_df is

Port (a : in STD_LOGIC;

b: out STD_LOGIC);

end NOTGATE_df;


architecture Dataflow of NOTGATE_df is

begin

b<= not a;

end Dataflow;

SCHEMATIC DIAGRAM :

 

TBW CODE :

entity NOTGATE_tbw is

-- Port ();

end NOTGATE_tbw;

architecture Dataflow of NOTGATE_df is

component NOTGATE_df is

Port (a : in STD_LOGIC;

b : out STD_LOGIC);

end component;

signal a1:STD_LOGIC='0';

signal b1:STD_LOGIC='0';

begin

uut:and_df port map(a=>a1,b=>b1);

stim_proc:process

begin

wait for 100 ns;


a1<='1';

wait ;

end process;

end Behavioral;

SIMULATION:

 

Nand GATE

VHD CODE

entity NAND_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end NAND_df;

architecture Dataflow of NAND_df is

begin

C<=A nand B;


```
end Dataflow;
```

Schematic Diagram



TEST BENCH CODE

```
entity NAND_df_TBW is
```

```
-- Port ( );
```

```
end NAND_df_TBW;
```

```
architecture Dataflow of NAND_df_TBW is
```

```
component NAND_df is
```

```
    Port ( A : in STD_LOGIC;
```

```
           B : in STD_LOGIC;
```

```
           C : out STD_LOGIC);
```

```
end component;
```

```
signal a1:STD_LOGIC := '0';
```

```
signal B1:STD_LOGIC := '0';
```

```
signal C1:STD_LOGIC;
```

```
begin
```

```
    uut:NAND_df Port Map(A=>a1,B=>b1,C=>c1);
```

```

stim_proc:process
begin
wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;

end Dataflow;

```

TEST BENCH WAVEFORM

 

NOR GATE

entity NOR_df is

```

Port ( A : in STD_LOGIC;

      B : in STD_LOGIC;

      C : out STD_LOGIC);
end NOR_df;

```

architecture Dataflow of NOR_df is

```

begin

C<=A nor B;

end Dataflow;

```

Schematic Diagram



TEST BENCH CODE

```

entity NOR_df_TBW is

-- Port ( );

end NOR_df_TBW;

```

architecture Dataflow of NOR_df_TBW is

component NOR_df is

```
Port ( A : in STD_LOGIC;
      B : in STD_LOGIC;
      C : out STD_LOGIC);
end component;

signal a1:STD_LOGIC :='0';
signal B1:STD_LOGIC :='0';
signal C1:STD_LOGIC;

begin

uut:NOR_df Port Map(A=>a1,B=>b1,C=>c1);

stim_process:process
begin
wait for 100 ns;

a1<='0';
b1<='0';


wait for 100 ns;

a1<='0';
b1<='1';

wait for 100 ns;

a1<='1';
b1<='0';

wait for 100 ns;


a1<='1';
b1<='1';

wait;
```

```
end process;
```

```
end Dataflow;
```

TEST BENCH WAVEFORM

 

XOR GATE

```
entity XOR_df is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : in STD_LOGIC;
```

```
          C : out STD_LOGIC);
```

```
end XOR_df;
```


```
architecture Dataflow of XOR_df is
```

```
begin
```

```
    C<=A XOR B;
```

```
end Dataflow;
```

Schematic Diagram

 

TEST BENCH CODE

entity XOR_df_TBW is

-- Port ();

end XOR_df_TBW;

architecture Dataflow of XOR_df_TBW is

component XOR_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC :='0';

signal c1:STD_LOGIC;

begin

uut:XOR_df Port Map(A=>a1,B=>b1,C=>c1);

stim_proc:process

begin

```

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';

b1<='1';

wait;

end process;

end Dataflow;

```

TEST BENCH WAVEFORM



XNOR GATE

entity XNOR_df is

Port (A : in STD_LOGIC;

```

    B : in STD_LOGIC;

    C : out STD_LOGIC);

end XNOR_df;

```

architecture Dataflow of XNOR_df is

```


begin

C<=A XNOR B;

end Dataflow;

```

Schematic Diagram

 

TEST BENCH CODE

```

entity XNOR_df_TBW is

-- Port ( );

end XNOR_df_TBW;

```

architecture Dataflow of XNOR_df_TBW is


```
component XNOR_df is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end component;

signal a1:STD_LOGIC :='0';
signal b1:STD_LOGIC :='0';
signal c1:STD_LOGIC;

begin

uut:XNOR_df Port Map(A=>a1,B=>b1,C=>c1);

stim_proc:process
begin
    wait for 100ns;

    a1<='0';
    b1<='0';

    wait for 100ns;

    a1<='0';
    b1<='1';

    wait for 100ns;

    a1<='1';
    b1<='0';

    wait for 100ns;


    a1<='1';
    b1<='1';

    wait;
```

```
end process;
```

```
end Dataflow;
```

TEST BENCH WAVEFORM

 

Day-2

Not using NAND

```
entity NOT_NAND_df is
```

```
    Port ( A : in STD_LOGIC;
```

```
          B : out STD_LOGIC);
```

```
end NOT_NAND_df;
```


```
architecture Dataflow of NOT_NAND_df is
```

```
begin
```

```
    B<=A nand A;
```

```
end Dataflow;
```

Schematic Diagram

 

TEST BENCH CODE

entity NOT_NAND_df_TBW is

-- Port ();

end NOT_NAND_df_TBW;

architecture Dataflow of NOT_NAND_df_TBW is

component NOT_NAND_df is

Port (A : in STD_LOGIC;

B : out STD_LOGIC);

end component;

signal A1:STD_LOGIC := '0';

signal B1:STD_LOGIC;

begin

uut:NOT_NAND_df Port Map(A=>a1,B=>b1);

stim_proc:process

begin

```
wait for 100ns;
```

```
a1<='0';
```

```
wait for 100ns;
```


```
a1<='1';
```

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TEST BENCH WAVEFORM

 

AND using NAND

```
entity AND_NAND_df is
```

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```
      C : out STD_LOGIC);
```

```
end AND_NAND_df;
```


```
architecture Dataflow of AND_NAND_df is
```

```
begin
```

```
C<=(A NAND B) NAND (A NAND B);
```

end Dataflow;

Schematic Diagram

 

TEST BENCH CODE

entity AND_NAND_df_TBW is

-- Port ();

end AND_NAND_df_TBW;

architecture Dataflow of AND_NAND_df_TBW is

component AND_NAND_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

signal A1:STD_LOGIC := '0';

signal B1:STD_LOGIC := '0';

signal C1:STD_LOGIC;

begin

uut:AND_NAND_df Port Map(A=>a1,B=>b1,C=>c1);

```
stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='1';
```

```
end process;
```

```
end Dataflow;
```

TEST BENCH WAVEFORM



OR using NAND

entity OR_NAND_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end OR_NAND_df;


architecture Dataflow of OR_NAND_df is

begin

C<=(A NAND A) NAND (B NAND B);

end Dataflow;

Schematic Diagram

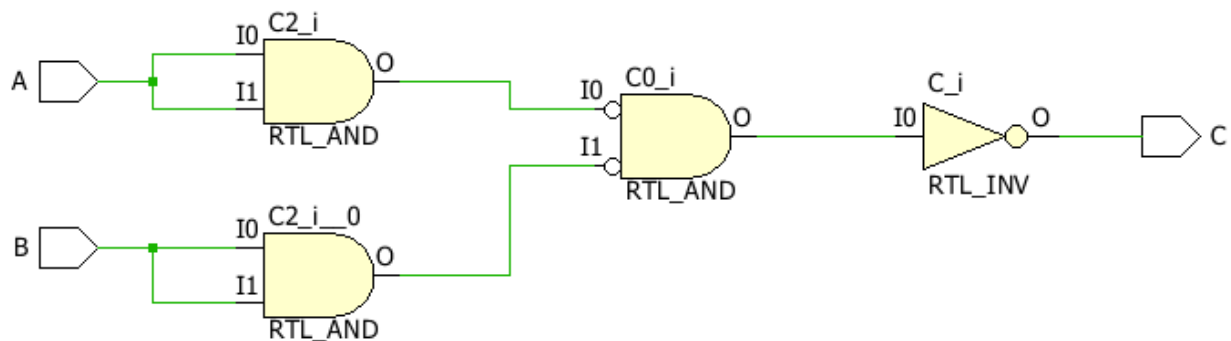

TEST BENCH CODE

entity OR_NAND_df_TBW is

-- Port ();

```
end OR_NAND_df_TBW;
```

architecture Dataflow of OR_NAND_df_TBW is

component OR_NAND_df is

```
    Port ( A : in STD_LOGIC;
```

```
          B : in STD_LOGIC;
```

```
          C : out STD_LOGIC);
```

```
end component;
```

```
signal A1:STD_LOGIC := '0';
```

```
signal B1:STD_LOGIC := '0';
```

```
signal C1:STD_LOGIC;
```

```
begin
```

```
uut:OR_NAND_df Port Map(A=>a1,B=>b1,C=>c1);
```

```
stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100ns;
```



```

a1<='1';

b1<='1';


wait;

end process;

end Dataflow;

```

TEST BENCH WAVEFORM

 

XOR using NAND

Vhdl code:

entity xor_nand is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end xor_nand;


architecture Behavioral of xor_nand is

begin

```
y<= (a nand (a nand b)) nand (b nand( a nand b));
```

```
end Behavioral;
```

Schematic Diagram:

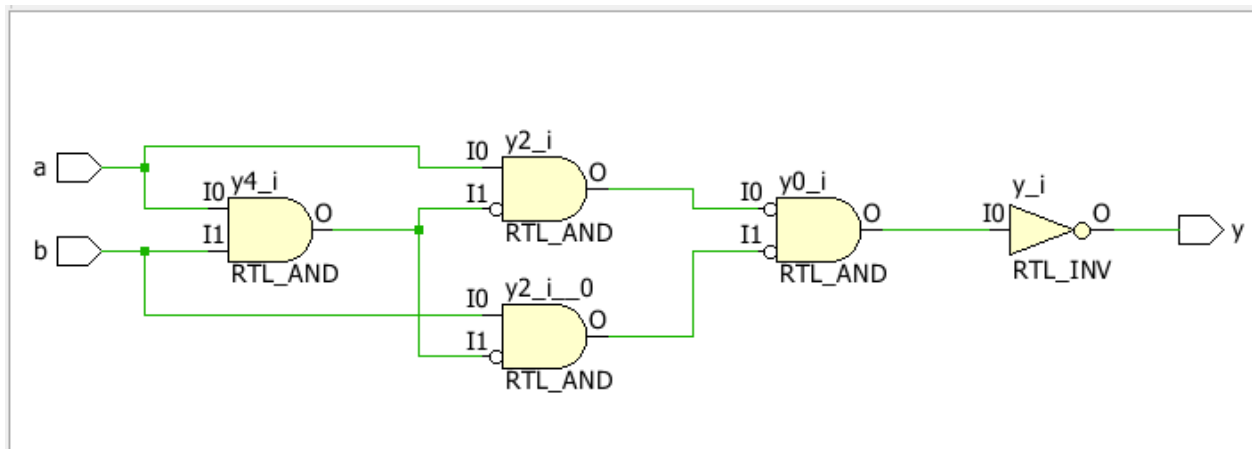

Tbw code:

```
entity xor_nand_tbw is
```

```
-- Port ( );
```

```
end xor_nand_tbw;
```

```
architecture Behavioral of xor_nand_tbw is
```

```
component xor_nand is
```

```
Port ( a : in STD_LOGIC;
```

```
      b : in STD_LOGIC;
```

```
      y : out STD_LOGIC);
```

```
end component;
```

```
signal a1:std_logic:='0';
signal b1:std_logic:='0';
signal y1:std_logic;

begin

uut:xor_nand port map(a=>a1,b=>b1,y=>y1);

stim_proc:process
begin
wait for 100 ns;

a1<='0';

b1<='1';

wait for 100 ns;

a1<='1';

b1<='0';

wait for 100 ns;

a1<='1';

b1<='1';

wait;

end process;

end Behavioral;
```

XNOR using NAND

Vhdl code:

```
entity xnor_nand is
```

```
    Port ( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          y : out STD_LOGIC);
```

```
end xnor_nand;
```


```
architecture Behavioral of xnor_nand is
```

```
begin
```

```
y<= ((a nand a) nand (b nand b)) nand (a nand b);
```

```
end Behavioral;
```

schematic Diagram:

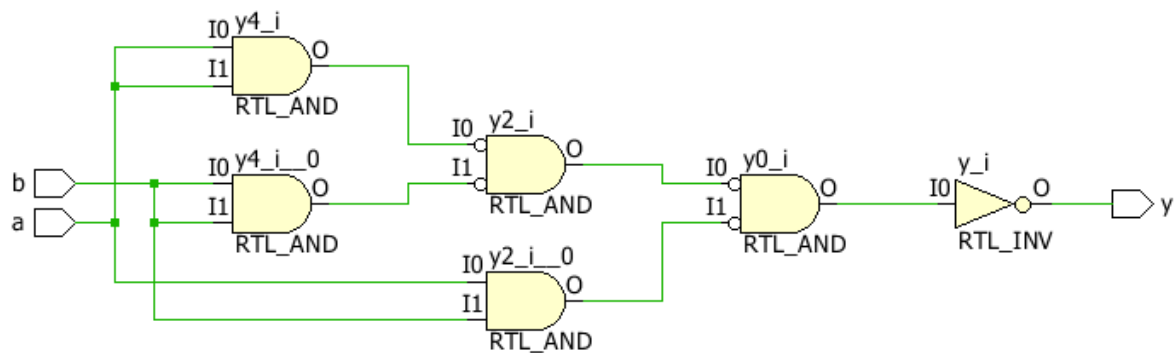

Tbw code:

entity xnor_nand_tbw is

-- Port ();

end xnor_nand_tbw;

architecture Behavioral of xnor_nand_tbw is

component xnor_nand is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end component;

signal a1:std_logic:='0';

```
signal b1:std_logic:='0';
```

```
signal y1:std_logic;
```

```
begin
```

```
uut:xnor_nand port map(a=>a1,b=>b1,y=>y1);
```

```
stim_proc:process
```

```
begin
```

```
wait for 100 ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100 ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100 ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

```
waveform:
```

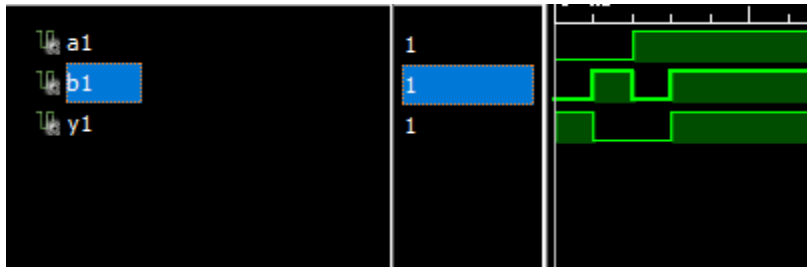

NOT using NOR

entity NOT_NOR_df is

Port (A : in STD_LOGIC;

B : out STD_LOGIC);

end NOT_NOR_df;


architecture Dataflow of NOT_NOR_df is

begin

B<=A NOR A;

end Dataflow;

Schematic Diagram

 

TEST BENCH CODE

```


entity NOT_NOR_df_TBW is
-- Port ( );
end NOT_NOR_df_TBW;

architecture Dataflow of NOT_NOR_df_TBW is
component NOT_NOR_df is
    Port ( A : in STD_LOGIC;
           B : out STD_LOGIC);
end component;
signal a1:STD_LOGIC := '0';
signal b1:STD_LOGIC;
begin
uut:NOT_NOR_df Port Map(A=>a1,B=>b1);
stim_proc:process
begin
wait for 100ns;
a1<='0';
wait for 100ns;
a1<='1';
wait;
end process;

end Dataflow;

```

TEST BENCH WAVEFORM

 

AND using NOR

entity AND_NOR_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end AND_NOR_df;


architecture Dataflow of AND_NOR_df is

begin

C<=(A NOR A) NOR (B NOR B);

end Dataflow;

Schematic Diagram

 

TEST BENCH CODE

entity AND_NOR_df_TBW is

```
-- Port ( );
```

```
end AND_NOR_df_TBW;
```

architecture Dataflow of AND_NOR_df_TBW is

component AND_NOR_df is

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```
      C : out STD_LOGIC);
```

```
end component;
```

```
signal a1:STD_LOGIC := '0';
```

```
signal b1:STD_LOGIC := '0';
```

```
signal c1:STD_LOGIC;
```

```
begin
```

```
uut:AND_NOR_df Port Map(A=>a1,B=>b1,C=>c1);
```

```
stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;

```

end Dataflow;

TEST BENCH WAVEFORM

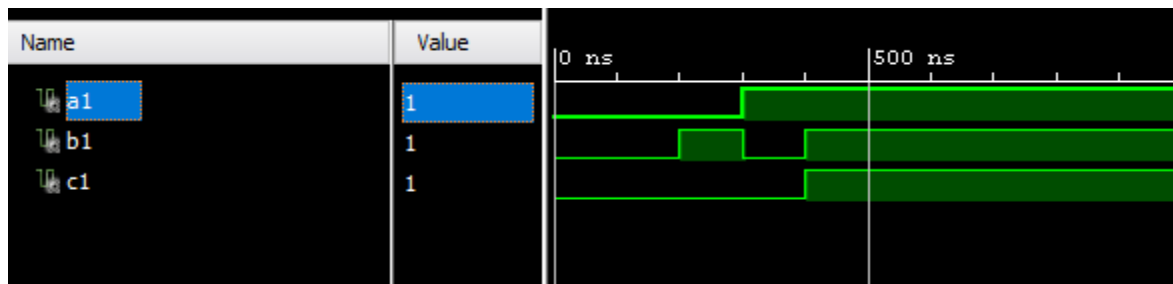

OR using NOR

entity OR_NOR_df is

Port (A : in STD_LOGIC;

```

    B : in STD_LOGIC;

    C : out STD_LOGIC);

end OR_NOR_df;

```


architecture Dataflow of OR_NOR_df is

```
begin
```

```
C<=(A NOR B) NOR (A NOR B);
```

```
end Dataflow;
```

Schematic Diagram

 

TEST BENCH CODE

```
entity OR_NOR_df_TBW is
```

```
-- Port ( );
```

```
end OR_NOR_df_TBW;
```

architecture Dataflow of OR_NOR_df_TBW is

```
component OR_NOR_df is
```

```
Port ( A : in STD_LOGIC;
```

```
B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC :='0';

signal c1:STD_LOGIC;

begin

uut:OR_NOR_df Port Map(A=>a1,B=>B1,C=>c1);

stim_proc:process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';wait for 100ns;

a1<='1';


b1<='1';

wait;

end process;

end Dataflow;
```

TEST BENCH WAVEFORM

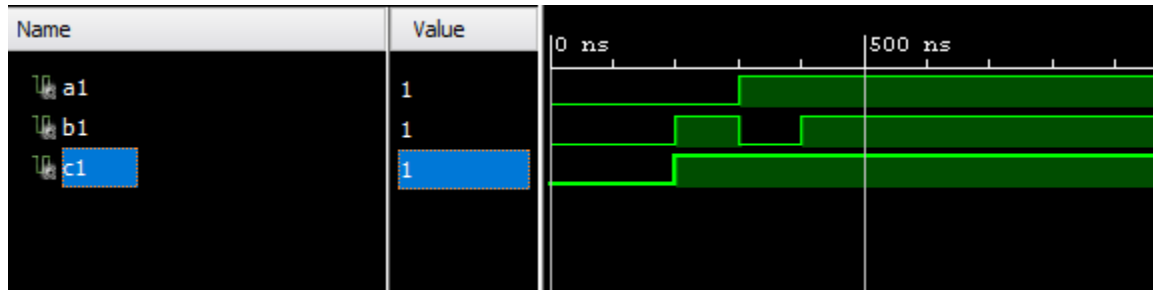

OR using NOR

entity AND_NOR_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end AND_NOR_df;

architecture Dataflow of AND_NOR_df is

begin

C<=(A NOR A) NOR (B NOR B);

end Dataflow;

tbw code:

architecture Dataflow of AND_NOR_df_TBW is

component AND_NOR_df is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC :='0';

signal c1:STD_LOGIC;

begin

uut:AND_NOR_df Port Map(A=>a1,B=>b1,C=>c1);

stim_proc:process

begin

wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';

wait for 100ns;

a1<='1';


b1<='1';

```
wait;
```

```
end process;
```

```
end Dataflow;
```

TEST BENCH WAVEFORM

 

IMPLEMENTATION OF OR GATE IN BEHAVIORAL MODE

VHDL code:

entity or_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end or_bv;

architecture Behavioral of or_bv is

begin

process(a,b)

begin

if(a='0' and b= '0') then

y<='0';

else


y<='1';

end if;

end process;

end Behavioral;

SCHEMATIC:

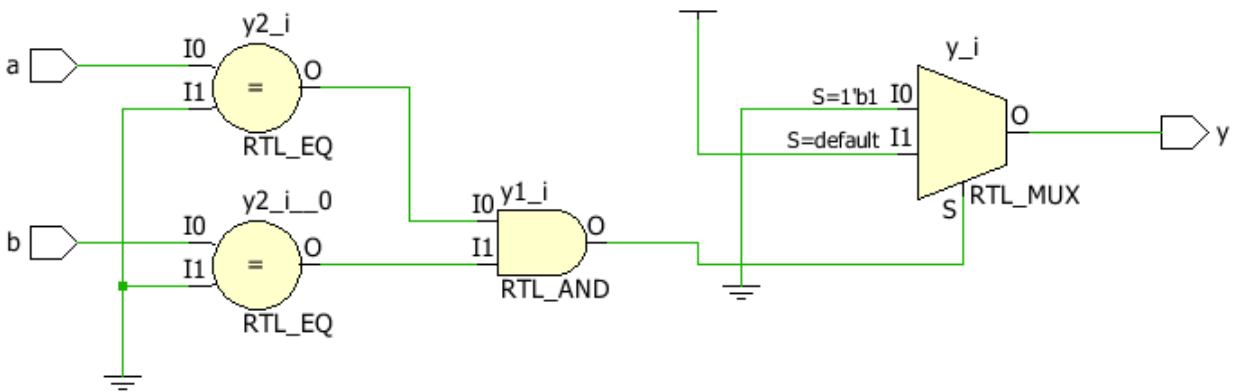

TBW CODE:

entity or_tbw is

-- Port ();

end or_tbw;

architecture Behavioral of or_tbw is

component or_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC :='0';

signal c1:STD_LOGIC;

begin

uut:or_bv Port Map(a=>a1,b=>b1,y=>c1);

```

stim_proc:process
begin
wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;

end Behavioral;

```

WAVEFORM:

 

IMPLEMENTATION OF AND GATE IN BEHAVIORAL MODE

VHDL CODE:

entity AND_DF is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end AND_DF;

architecture Behavioral of AND_DF is

begin

process(a,b)

begin if(a='1' and b='1')then

y<='1';

else


y<='0';

end if;

end process;

end Behavioral;

schematic:

 

Tbw code:

entity and_bv_tbw is

-- Port ();

end and_bv_tbw;

architecture Behavioral of and_bv_tbw is

component AND_DF is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

y : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC :='0';

signal c1:STD_LOGIC;

begin

uut:AND_DF Port Map(a=>a1,b=>b1,y=>c1);

```

stim_proc:process
begin
wait for 100ns;

a1<='0';

b1<='0';

wait for 100ns;

a1<='0';

b1<='1';

wait for 100ns;

a1<='1';

b1<='0';wait for 100ns;

a1<='1';

b1<='1';


wait;

end process;

end Behavioral;

```

wave form:

 

IMPLEMENTATION OF NOT GATE IN BEHAVIORAL MODE

VHDL CODE:

entity NOT_BV is

Port (a : in STD_LOGIC;

b : out STD_LOGIC);

end NOT_BV;

architecture Behavioral of NOT_BV is

begin

process(a)

begin

if(a='0')then

b<='1';

else


b<='0';

end if;

end process;

end Behavioral;

SCHEMATIC:

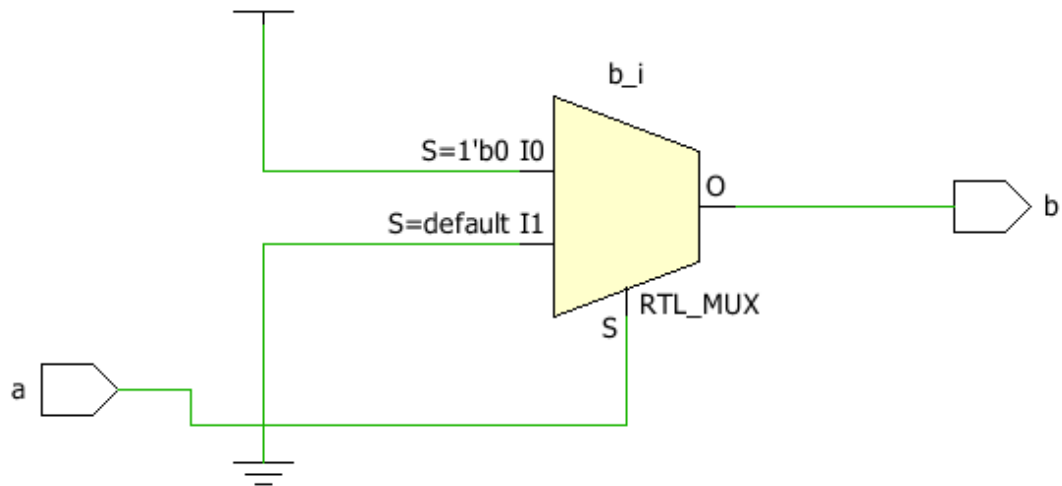

TBW CODE:

entity NOT_DF_TBW is

-- Port ();

end NOT_DF_TBW;

architecture Behavioral of NOT_DF_TBW is

component NOT_BV is

Port (a : in STD_LOGIC;

b : out STD_LOGIC);

end component;

signal a1:STD_LOGIC :='0';

signal b1:STD_LOGIC;

begin

uut:NOT_BV Port Map(a=>a1,b=>b1);


```
stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
a1<='0';
```

```
wait for 100ns;
```


```
a1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

WAVEFORM:

 

IMPLEMENTATION OF NAND Gate IN BEHAVIORAL MODE

Truth Table:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

VHDL Code

entity nand_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end nand_bv;

architecture Behavioral of nand_bv is

begin

process(a,b)

begin

if(a='1' AND b='1') then

c<='0';

else

```

    c<='1';


end if;

end process;

end Behavioral;

```

SCHEMATIC

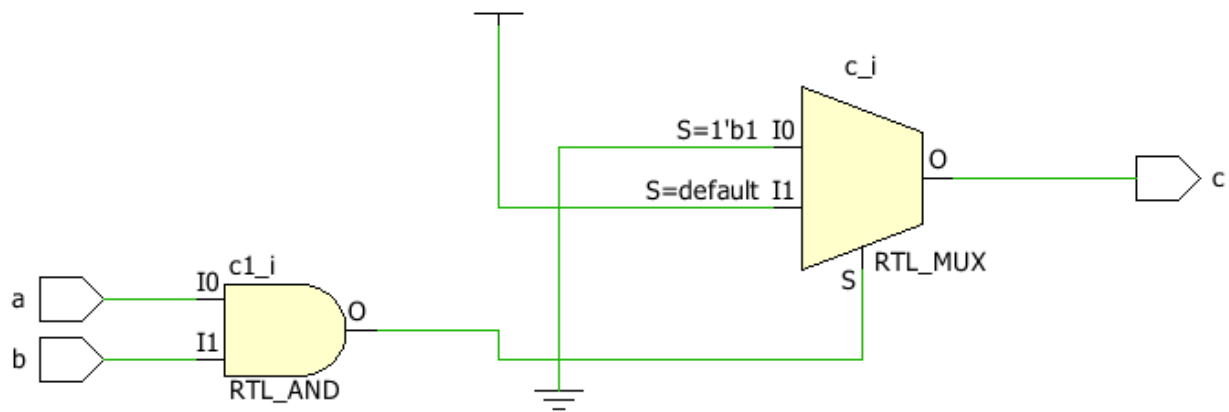

TBW Code

architecture Behavioral of nand_bv_tbw is

component nand_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

```
begin

uut: nand_bv port map(a=>a1,b=>b1,c=>c1);

stim_proc: process

begin

wait for 100 ns;

a1<='0';

b1<='0';


wait for 100 ns;

a1<='0';

b1<='1';


wait for 100 ns;

a1<='1';

b1<='0';


wait for 100 ns;

a1<='1';


b1<='1';

wait;


end process;

end Behavioral;
```

Waveform

 

IMPLEMENTATION OF NOR Gate IN BEHAVIORIAL MODE

Truth Table:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

VHDL Code

architecture Behavioral of nor_bv is

begin

process(a,b)

begin

if(a='0' AND b='0') then

c<='1';

else


c<='0';

end if;

end process;

end Behavioral;

SCHEMATIC

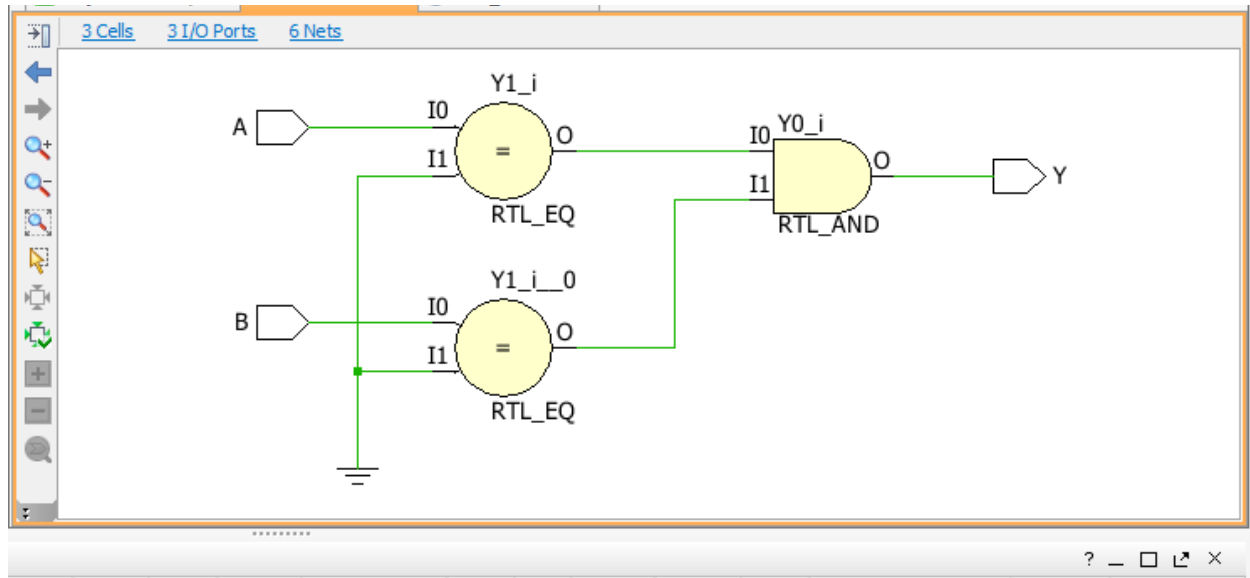

TBW Code

architecture Behavioral of nor_bv_tbw is

component nor_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

```
uut: nor_bv port map(a=>a1,b=>b1,c=>c1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100 ns;
```

```
a1<='0';
```

```
b1<='0';
```

```
wait for 100 ns;
```

```
a1<='0';
```

```
b1<='1';
```

```
wait for 100 ns;
```

```
a1<='1';
```

```
b1<='0';
```

```
wait for 100 ns;
```

```
a1<='1';
```


```
b1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

Waveform

 

IMPLEMENTATION OF XOR Gate IN BEHAVIORIAL MODE

VHDL Code

entity xor_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end xor_bv;

architecture Behavioral of xor_bv is

begin

process(a,b)

begin

if(a=b) then

c<='0';

else


c<='1';

end if;

end process;

end Behavioral;

SCHEMATIC

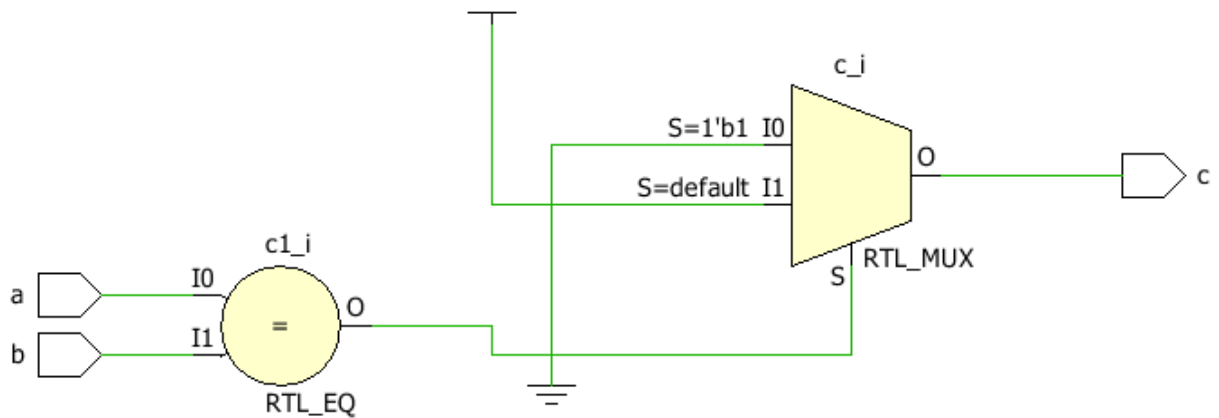

TBW Code

entity xor_bv_tbw is

-- Port ();

end xor_bv_tbw;

architecture Behavioral of xor_bv_tbw is

component xor_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal a1:STD_LOGIC:= '0';

Signal b1:STD_LOGIC:= '0';

```
Signal c1:STD_LOGIC;

begin

uut: xor_bv port map(a=>a1,b=>b1,c=>c1);

stim_proc: process

begin

wait for 100 ns;

a1<='0';

b1<='0';


wait for 100 ns;

a1<='0';

b1<='1';


wait for 100 ns;

a1<='1';

b1<='0';


wait for 100 ns;

a1<='1';


b1<='1';

wait;

end process;

end Behavioral;
```

Waveform

 

IMPLEMENTATION OF XNOR Gate IN BEHAVIORAL MODE

Truth Table:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

VHDL Code

entity xnor_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end xnor_bv;

architecture Behavioral of xnor_bv is

begin

process(a,b)

```

begin
if(a=b) then

    c<='1';

else


    c<='0';

end if;

end process;

```

end Behavioral;

 

TBW Code

architecture Behavioral of xnor_bv_tbw is

component xnor_bv is

```

Port ( a : in STD_LOGIC;
      b : in STD_LOGIC;
      c : out STD_LOGIC);

```

```
end component;

Signal a1:STD_LOGIC:='0';

Signal b1:STD_LOGIC:='0';

Signal c1:STD_LOGIC;

begin

uut: xnor_bv port map(a=>a1,b=>b1,c=>c1);

stim_proc: process

begin

wait for 100 ns;

a1<='0';

b1<='0';


wait for 100 ns;

a1<='0';

b1<='1';


wait for 100 ns;

a1<='1';

b1<='0';


wait for 100 ns;

a1<='1';

b1<='1';

wait;
```

```
end process;  
  
end Behavioral;
```

Waveform



Half Adder Behavioral


VHD Code

```
entity half_adder_df is  
    Port ( a : in STD_LOGIC;  
           b : in STD_LOGIC;  
           s : out STD_LOGIC;  
           c : out STD_LOGIC);  
end half_adder_df;  
  
architecture Behavioral of half_adder_df is  
  
begin
```

```
process(a, b)
begin
if(a = b) then
    s <= '0';
else
    s <= '1';
end if;
if(a = '1' and b='1') then
    c <= '1';
else
    c <= '0';
end if;
end process;
```

end Behavioral;

Schematic Diagram

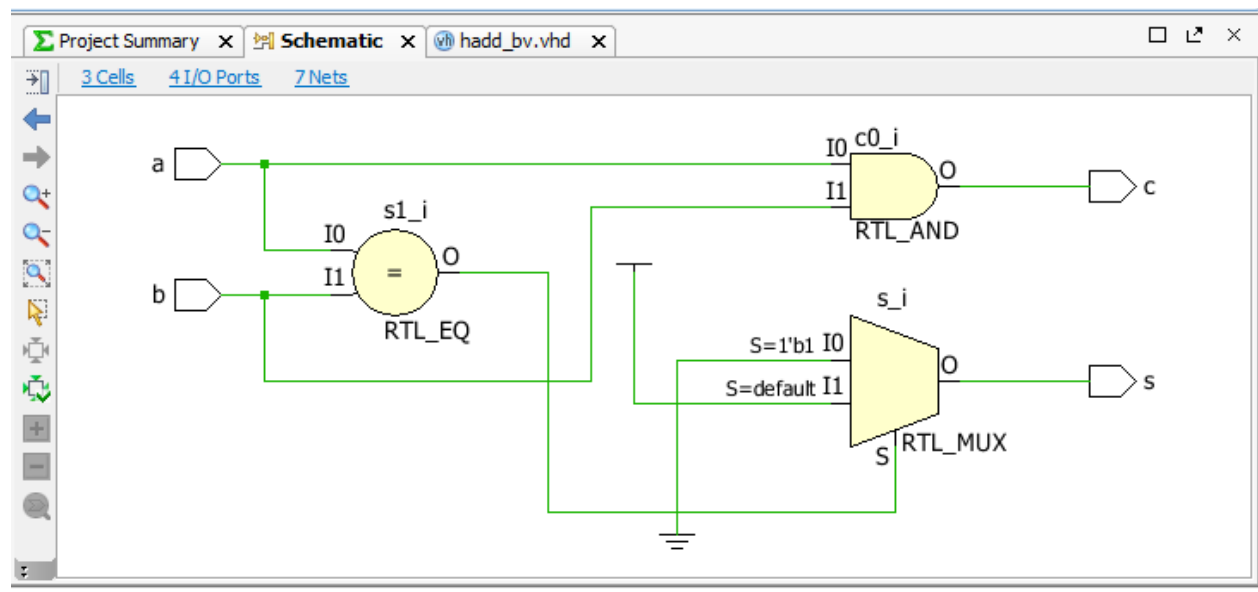

Test Bench Code

entity half_adder_df_tbw is

-- Port ();

end half_adder_df_tbw;

architecture Behavioral of half_adder_df_tbw is

component half_adder_df is

Port (a : in STD_LOGIC;


b : in STD_LOGIC;

s : out STD_LOGIC;


```
        c : out STD_LOGIC);  
end component;  
  
Signal a1: STD_LOGIC := '0';  
Signal b1: STD_LOGIC := '0';  
Signal s1: STD_LOGIC;  
Signal c1: STD_LOGIC;  
begin  
    uut: half_adder_df port map (a=>a1, b=>b1, s=>s1, c=>c1);  
    stim_proc: process  
    begin  
        wait for 100ns;  
        a1 <= '0';  
        b1 <= '0';  
        wait for 100ns;  
        a1 <= '0';  
        b1 <= '1';  
        wait for 100ns;
```

```
a1 <= '1';  
b1 <= '0';  
wait for 100ns;  
a1 <= '1';  
b1 <= '1';  
wait;  
end process;  
end Behavioral;
```

Test Bench Waveform

 

Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder Behavioral

VHD Code

entity fadd_bv is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

q : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end fadd_bv;

architecture Behavioral of fadd_bv is

begin

process(a,b,q)

begin

if(a = '0')then

if(b = q)then

s <= '0';

else

s <= '1';

end if;

if(b = '1' AND q = '1')then

c <= '1';

else

c <= '0';

end if;

end if;

if(a = '1')then

if(b = q)then

s <= '1';

else

s <= '0';

end if;

if(b = '1' OR q = '1')then

c <= '1';

else

c <= '0';


end if;

end if;

end process;

end Behavioral;

Schematic Diagram

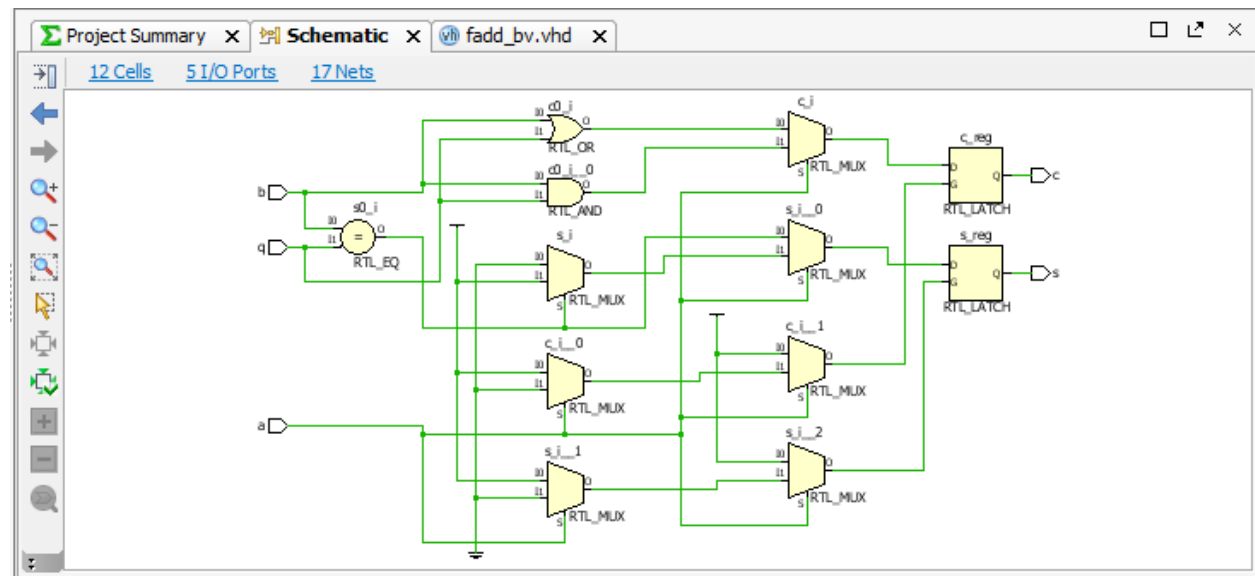

Test Bench Code

entity fadd_bv_tbw is

-- Port ();

end fadd_bv_tbw;

architecture Behavioral of fadd_bv_tbw is

component fadd_bv is

Port (a : in STD_LOGIC;

 b : in STD_LOGIC;

 q : in STD_LOGIC;

 s : out STD_LOGIC;

 c : out STD_LOGIC);

end component;

Signal a1: STD_LOGIC := '0';

Signal b1: STD_LOGIC := '0';

Signal q1: STD_LOGIC := '0';

```
Signal s1: STD_LOGIC;
```

```
Signal c1: STD_LOGIC;
```

```
begin
```

```
uut:fadd_bv Port Map(a=>a1,b=>b1,q=>q1,s=>s1,c=>c1);
```

```
stim_proc:process
```

```
begin
```

```
    wait for 50 ns;
```

```
    a1 <= '0';
```

```
    b1 <= '0';
```

```
    q1 <= '0';
```

```
    wait for 50ns;
```

```
    a1 <= '0';
```

```
    b1 <= '0';
```

```
    q1 <= '1';
```

```
    wait for 50ns;
```

```
    a1 <= '0';
```

```
    b1 <= '1';
```

```
    q1 <= '0';
```


wait for 50ns;

a1 <= '0';

b1 <= '1';

q1 <= '1';

wait for 50ns;

a1 <= '1';

b1 <= '0';

q1 <= '0';

wait for 50ns;

a1 <= '1';

b1 <= '0';

q1 <= '1';

wait for 50ns;

a1 <= '1';

b1 <= '1';

q1 <= '0';

wait for 50ns;

```
a1 <= '1';
```

```
b1 <= '1';
```


```
q1 <= '1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

Test Bench Waveform

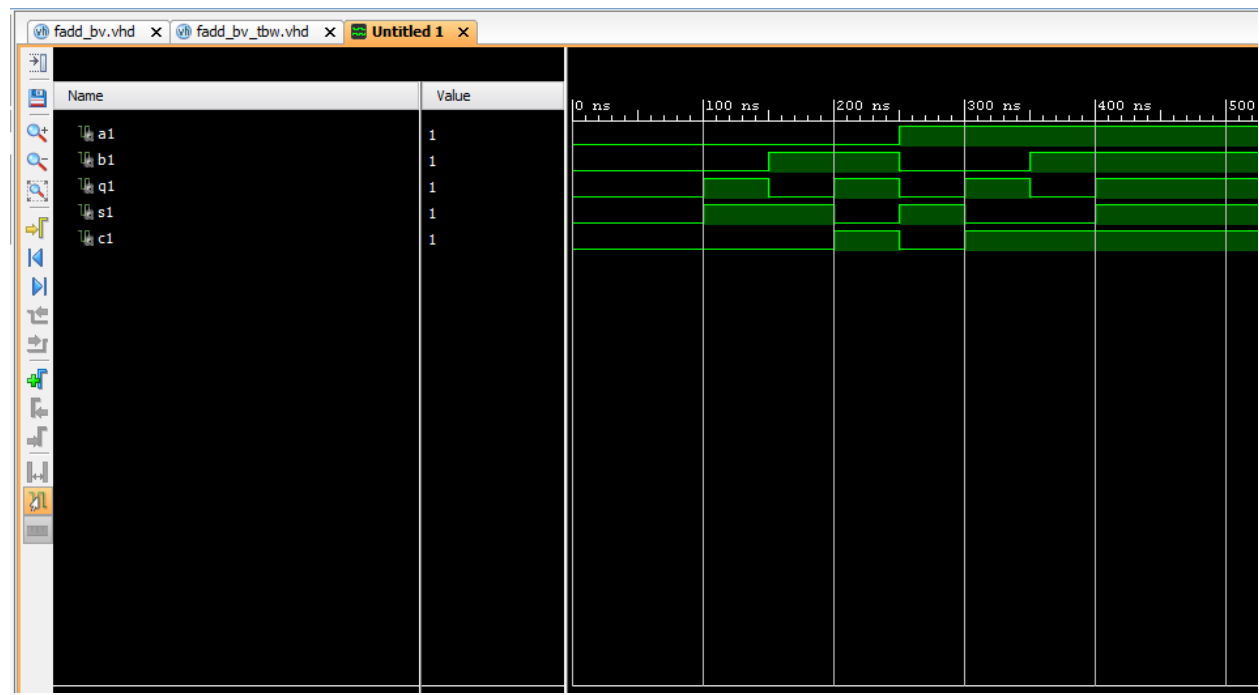

Truth Table

A	B	Q	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder [Structural]

VHD Code

entity fa_struc is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : in STD_LOGIC;

sum : out STD_LOGIC;

carry : out STD_LOGIC);

end fa_struc;

architecture structural of fa_struc is

component half_adder_df is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end component;

component or_df is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

c : out STD_LOGIC);

end component;

Signal c1, c2, s1 : std_logic;

begin


l1:half_adder_df Port Map(a, b, s1, c1);

l2:half_adder_df Port Map(s1, c, sum, c2);

l3:or_df Port Map(c1, c2, carry);

end structural;

Schematic Diagram

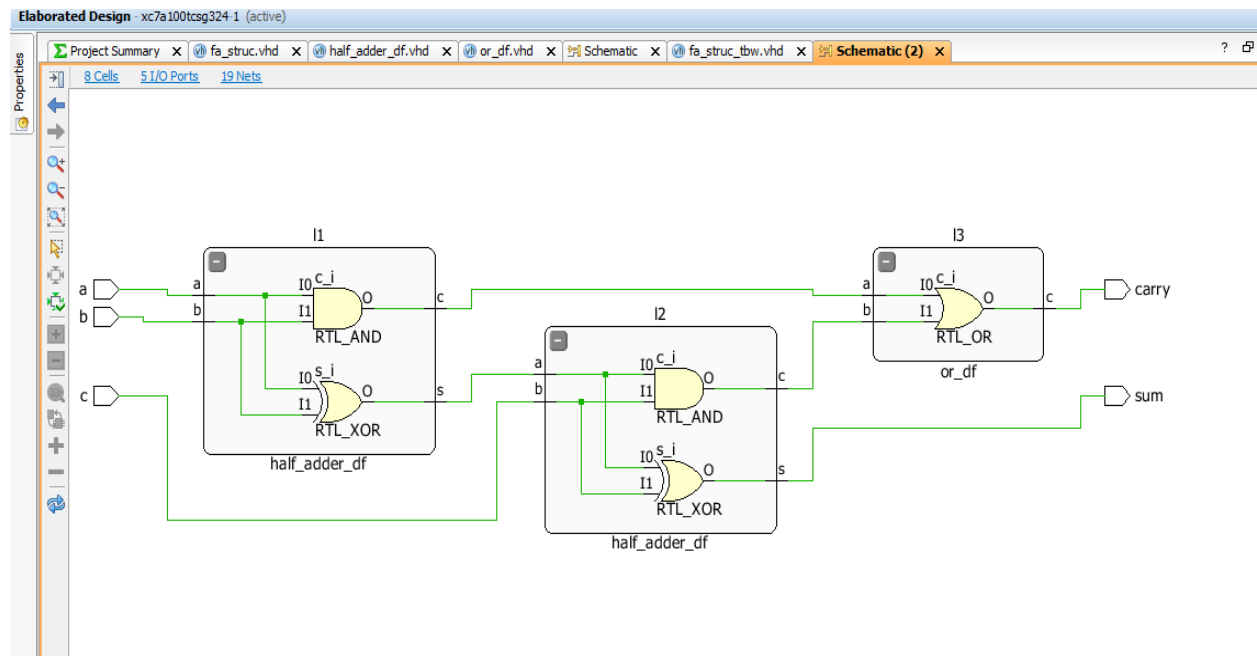

Test Bench Code

entity fa_struc_tbw is

-- Port ();

end fa_struc_tbw;

architecture Behavioral of fa_struc_tbw is

```
component fa_struct is
Port ( a : in STD_LOGIC;
      b : in STD_LOGIC;
      c : in STD_LOGIC;
      sum : out STD_LOGIC;
      carry : out STD_LOGIC);
end component;
```

```
Signal a1: STD_LOGIC := '0';
Signal b1: STD_LOGIC := '0';
Signal c1: STD_LOGIC := '0';
Signal sum1: STD_LOGIC;
Signal carry1: STD_LOGIC;
begin
uut:fa_struct Port
Map(a=>a1,b=>b1,c=>c1,sum=>sum1,carry=>carry1);
stim_proc:process
begin
```

wait for 50 ns;

a1 <= '0';

b1 <= '0';

c1 <= '0';

wait for 50ns;

a1 <= '0';

b1 <= '0';

c1 <= '1';

wait for 50ns;

a1 <= '0';

b1 <= '1';

c1 <= '0';

wait for 50ns;

a1 <= '0';

b1 <= '1';


c1 <= '1';

wait for 50ns;


```
a1 <= '1';  
b1 <= '0';  
c1 <= '0';  
wait for 50ns;  
a1 <= '1';  
b1 <= '0';  
c1 <= '1';  
wait for 50ns;  
a1 <= '1';  
b1 <= '1';  
c1 <= '0';  
wait for 50ns;  
a1 <= '1';  
b1 <= '1';  
c1 <= '1';  
  
wait;  
end process;
```

end Behavioral;

Test Bench Waveform

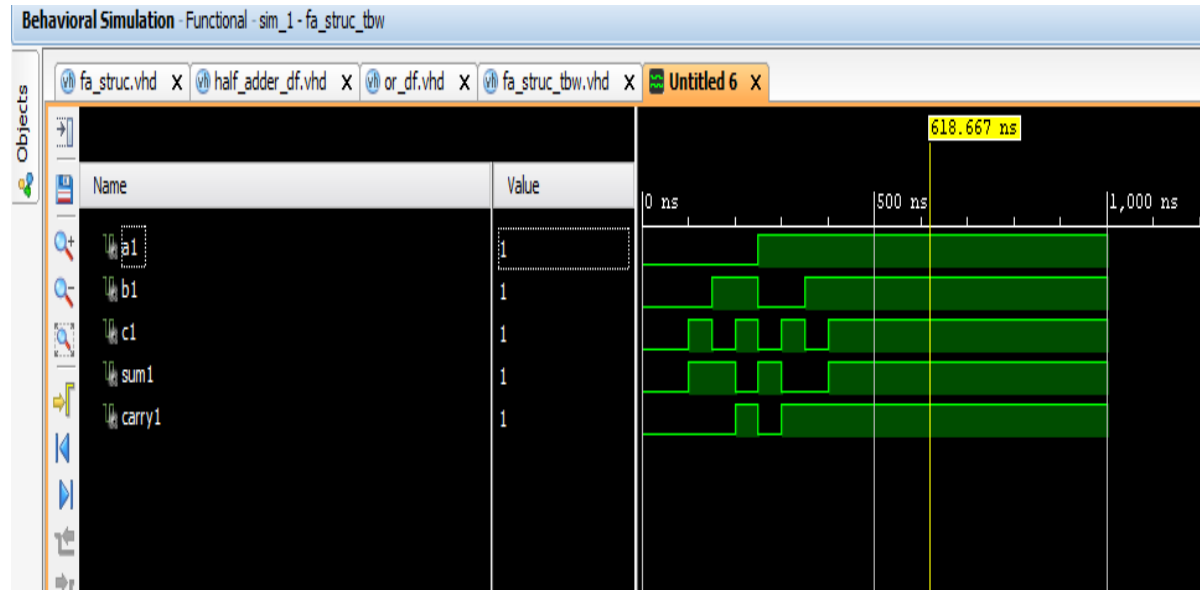

ALU Behavioral (03/04/2025)

VHD Code

entity alu_bv is

Port (a : in unsigned (3 downto 0);

b : in unsigned (3 downto 0);

ch : in STD_LOGIC_VECTOR (2 downto 0);

res : out unsigned (3 downto 0));

end alu_bv;

architecture Behavioral of alu_bv is

begin

process(a, b, ch)

begin

case ch is

when "000" => res <= a+b;

when "001" => res <= a-b;

when "010" => res <= a+1;

when "011" => res <= a-1;

when "100" => res <= a and b;

when "101" => res <= a or b;

when "110" => res <= not a;

when "111" => res <= a xor b;


when others => NULL;

end case;

end process;

end Behavioral;

Schematic Diagram

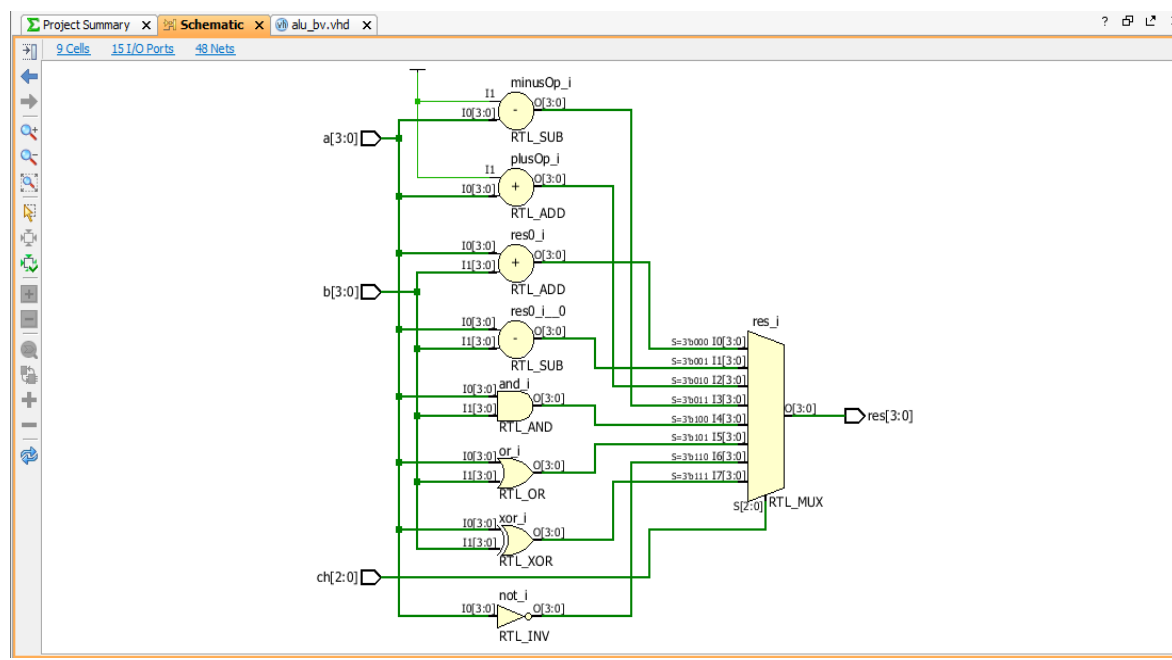

Test Bench Code

entity alu_bv_tbw is

-- Port ();

end alu_bv_tbw;

architecture Behavioral of alu_bv_tbw is

component alu_bv is

Port (a:in unsigned (3 downto 0);

b:in unsigned (3 downto 0);

s:in STD_LOGIC_VECTOR (2 downto 0);

r:out unsigned (3 downto 0));

end component;

Signal a1:unsigned(3 downto 0):="1001";

Signal b1:unsigned(3 downto 0):="1100";

Signal sol:STD_LOGIC_VECTOR(2 downto 0):="000";

Signal r1:unsigned(3 downto 0);

begin

uut:alu_bv port map(a=>a1, b=>b1, s=>sol, r=>r1);

stim_proc: process

begin

wait for 100ns;

sol<="000";

wait for 100ns;

```
sol<="001";  
wait for 100ns;  
sol<="010";  
wait for 100ns;  
sol<="011";  
wait for 100ns;  
sol<="100";  
wait for 100ns;  
sol<="101";  
wait for 100ns;  
sol<="110";  
wait for 100ns;  
sol<="111";  
wait;  
end process;
```

```
end Behavioral;
```

Test Bench Waveform

